
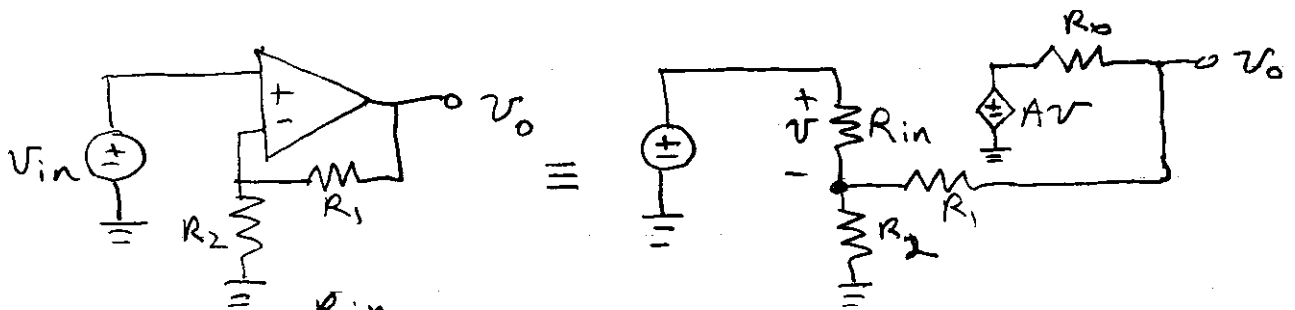


EE 5345 HW 1 - SOLUTIONS

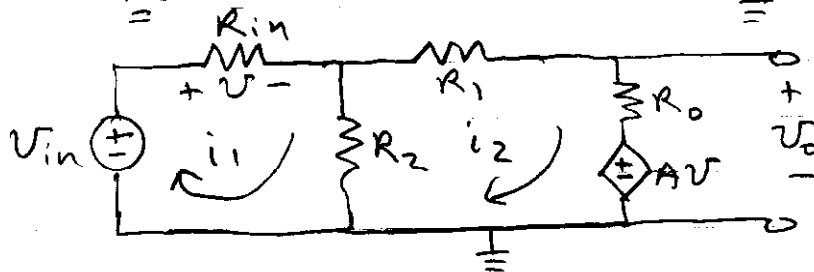

OR:



LOOP ANALYSIS:

$$\textcircled{1} \quad V_{in} = i_1(R_{in} + R_2) - i_2 R_2$$

$$0 = -i_1 R_2 + i_2(R_2 + R_1 + R_0) + A i_1 R_{in}$$

$$\textcircled{2} \quad 0 = i_1(A R_{in} - R_2) + i_2(R_2 + R_1 + R_0)$$

$$i_1 = \frac{\begin{vmatrix} V_{in} & -R_2 \\ 0 & R_2 + R_1 + R_0 \end{vmatrix}}{\begin{vmatrix} R_{in} + R_2 & -R_2 \\ A R_{in} - R_2 & R_2 + R_1 + R_0 \end{vmatrix}} \quad \beta = \frac{R_2}{R_1 + R_2}$$

$$= \frac{V_{in}(R_2 + R_1 + R_0)}{(R_{in} + R_2)(R_2 + R_1 + R_0) + R_2(A R_{in} - R_2)}$$

$$Z_{in} = \frac{V_{in}}{i_1} = \frac{(R_{in} + R_2)(R_2 + R_1 + R_0) + R_2(A R_{in} - R_2)}{R_2 + R_1 + R_0}$$

$$= (R_{in} + R_2) + \frac{R_2(A R_{in} - R_2)}{R_2 + R_1 + R_0}$$

$$= R_{in} \left[1 + \frac{A R_2}{R_1 + R_2 + R_0} \right] + R_2 - \frac{R_2^2}{R_1 + R_2 + R_0}$$

$$\approx R_{in}(1 + A\beta)$$

small compared to 1st term

$$Z_{out} = \frac{V_{oc}}{i_{sc}}, \quad V_{oc} = i_2 R_o + AV$$

$$= i_2 R_o + A i_1 R_{in}$$

$$i_2 = \frac{\begin{vmatrix} R_{in} + R_2 & V_{in} \\ AR_{in} - R_2 & 0 \end{vmatrix}}{\dots}$$


| etc. |

$$= \frac{-V_{in}(AR_{in} - R_2)}{(R_{in} + R_2)(R_1 + R_2 + R_o) + R_2(AR_{in} - R_2)}$$

$$V_{oc} = \frac{-V_{in} R_o (AR_{in} - R_2) + AR_{in} V_{in} (R_1 + R_2 + R_o)}{(R_{in} + R_2)(R_1 + R_2 + R_o) + R_2(AR_{in} - R_2)}$$

$$= \frac{AR_{in} V_{in} (R_1 + R_2) + V_{in} R_o R_2}{(R_{in} + R_2)(R_1 + R_2 + R_o) + R_2(AR_{in} - R_2)}$$

TO GET i_{sc} :

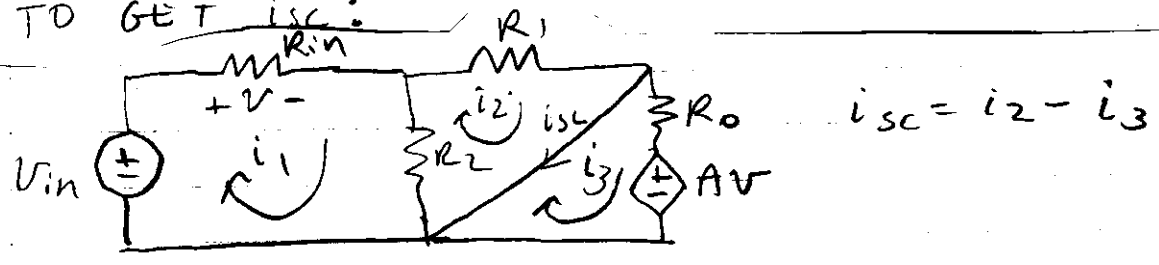

LOOP 1: $V_{in} = i_1(R_{in} + R_2) - i_2 R_2$

LOOP 2: $0 = -i_1 R_2 + i_2(R_1 + R_2)$

LOOP 3: $0 = i_3 R_o + AR_{in} i_1 = i_1 AR_{in} + i_3 R_o$

$$i_2 = \frac{\begin{vmatrix} (R_{in} + R_2) & V_{in} & 0 \\ -R_2 & 0 & 0 \\ AR_{in} & 0 & R_o \end{vmatrix}}{\dots} = 0$$

$$= \frac{R_o R_2 V_{in}}{R_o (R_{in} + R_2) (R_1 + R_2)} \approx 0$$

$$i_s = \frac{\begin{vmatrix} (R_1 + R_2) & -R_2 & V_{in} \\ 0 & (R_1 + R_2) & 0 \\ A R_{in} & 0 & 0 \end{vmatrix}}{\begin{vmatrix} (R_1 + R_2) & -R_2 & 0 \\ 0 & (R_1 + R_2) & 0 \\ A R_{in} & 0 & R_0 \end{vmatrix}} = -i_{sc}$$

$$= \frac{+V_{in} A R_{in} (R_1 + R_2)}{R_0 [(R_1 + R_2)(R_1 + R_2)]}$$

$$Z_{out} = \frac{V_{oc}}{i_{sc}} = \frac{[A R_{in} V_{in} (R_1 + R_2) + V_{in} R_0 R_2] R_0 (R_1 + R_2)}{V_{in} A R_{in} [(R_1 + R_2)(R_1 + R_2 + R_0) + R_2 (A R_{in} - R_2)]}$$



$$\doteq \frac{A R_{in} (R_1 + R_2) (R_1 + R_2) R_0}{A R_{in} (R_1 + R_2) (R_1 + R_2) + A^2 R_{in}^2 R_2}$$

$$= \frac{R_0}{1 + \frac{R_2 A R_{in}}{(R_1 + R_2)(R_1 + R_2)}}, \quad R_2 \ll R_{in}$$

$$\approx \frac{R_0}{1 + \beta A}$$

NOTE NON-INVERTING AMP ONLY APPROXIMATES IDEAL TYPE-I FEEDBACK RELATIONSHIPS FOR $Z_{in} + Z_{out}$. THIS IS DUE TO THE β NETWORK HAVING FINITE INPUT IMPEDANCE.

2.

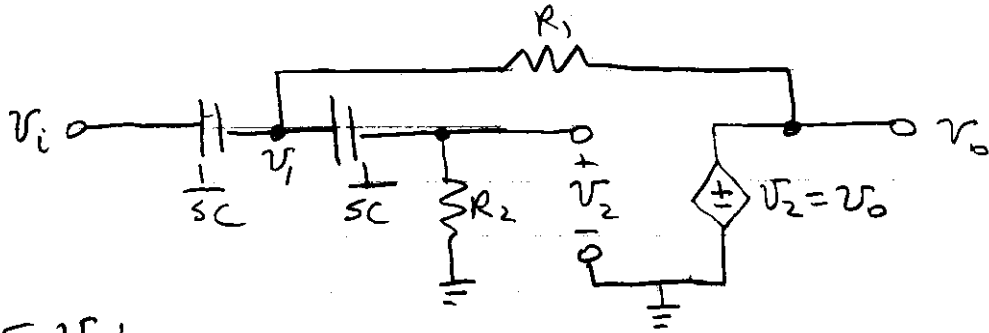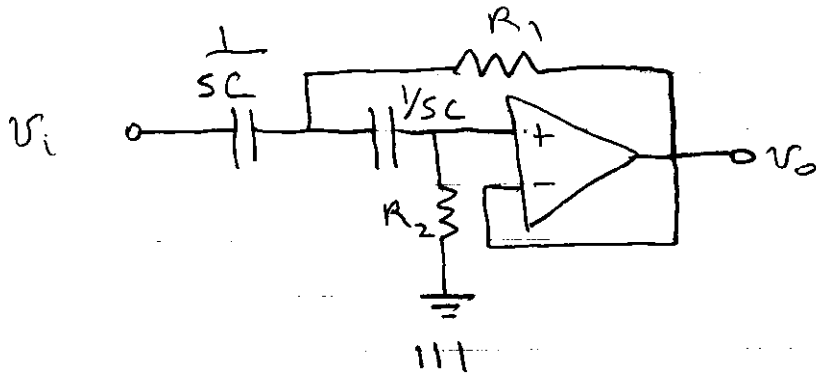

NODE \$v_1\$:

$$(v_i - v_1)SC = \frac{v_1 - v_2}{R_1} + (v_1 - v_2)SC$$

$$v_i SC = v_1 \left(\frac{1}{R_1} + 2SC \right) + v_2 \left(-\frac{1}{R_1} - SC \right) \quad (1)$$

NODE \$v_2\$:

$$(v_1 - v_2)SC = v_2 / R_2$$

$$0 = v_1 SC + v_2 \left(-SC - 1/R_2 \right) \quad (2)$$

$$v_2 = \frac{\begin{vmatrix} (2SC + 1/R_1) & v_i SC \\ SC & 0 \end{vmatrix}}{\begin{vmatrix} (2SC + 1/R_1) & -(SC + 1/R_1) \\ SC & -(SC + 1/R_2) \end{vmatrix}} = v_o$$

$$= \frac{+ v_i SC^2}{+ (2SC + 1/R_1)(SC + 1/R_2) - SC(SC + 1/R_1)}$$

$$\frac{v_o}{v_i} = \frac{S^2 C^2}{-S^2 C^2 - \frac{SC}{R_1} + 2S^2 C^2 + \frac{SC}{R_1} + \frac{2SC}{R_2} + \frac{1}{R_1 R_2}}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{2}{sCR_2} + \frac{1}{s^2R_1R_2C^2}} = H(s)$$

CHECK:

IF WE SUBSTITUTE:


$$R_1 = \frac{1}{\sqrt{2}CR_2}, \quad R_2 = \frac{\sqrt{2}}{C\omega_c}$$

GET:

$$= \frac{1}{1 + \frac{2}{s\sqrt{2}/C\omega_c} + \frac{1}{s^2C^2/\omega_c^2R_2^2}} = \frac{1}{1 + \frac{\sqrt{2}}{(s/\omega_c)} + \frac{1}{s^2/\omega_c^2}} \quad \checkmark$$

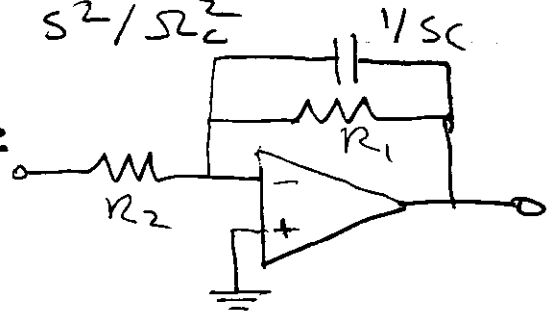3. FIRST-ORDER BUTTERWORTH:

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_1/sC}{R_2 + R_1 + 1/sC}$$



$$= \frac{-R_1/R_2}{1 + sR_1C} = \frac{K}{1 + (s/\omega_c)} = \frac{K}{B_1(\frac{s}{\omega_c})}$$

$$\omega_c = \frac{1}{R_1C}, \quad K = -R_1/R_2, \quad \uparrow \text{ HAS FORM OF } B_1$$

4,

R_f	R_g	R_1	R_2	(K)	CMRR (dB)
9.5	9.5	0.95	0.95		∞
9.5	9.5	0.95	1.05		40.42
9.5	9.5	1.05	0.95		40.42
9.5	9.5	1.05	1.05		∞
9.5	10.5	0.95	0.95		41.21
9.5	10.5	0.95	1.05		∞
9.5	10.5	1.05	0.95		34.79 ←
9.5	10.5	1.05	1.05		40.42
10.5	9.5	0.95	0.95		41.21
10.5	9.5	0.95	1.05		34.79 ←
10.5	9.5	1.05	0.95		∞
10.5	9.5	1.05	1.05		40.42
10.5	10.5	0.95	0.95		315.88
10.5	10.5	0.95	1.05		41.21
10.5	10.5	1.05	0.95		41.21
10.5	10.5	1.05	1.05		∞