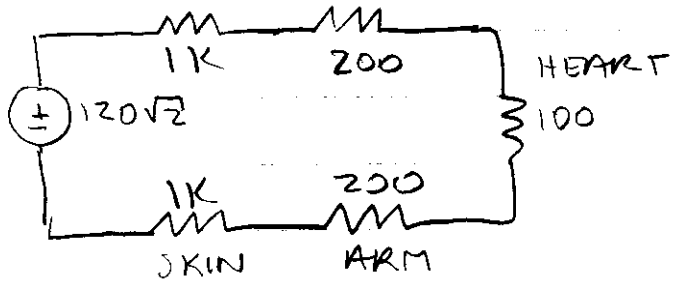


SOLUTIONS 14.1, 14.6, 14.9, 14.13, 14.17

14.1



$$I = \frac{120\sqrt{2}}{2K + 500} = 67 \text{ mA}, \text{ see also FIG. 14.1}$$


75 mA is typical.

assume a $10 \times 10 \text{ cm}$ c.s. area: $\frac{75 \text{ mA}}{100 \text{ cm}^2}$


LOWEST THRESHOLD CURRENT DENSITY = 0.75 mA/cm^2

$$1000 \text{ mA} / 100 \text{ mm}^2 \times \frac{1 \text{ mA}}{10^3 \text{ mA}} \times \frac{10^2 \text{ mm}^2}{1 \text{ cm}^2} = 1 \text{ mA/cm}^2 \approx \text{SAME}$$

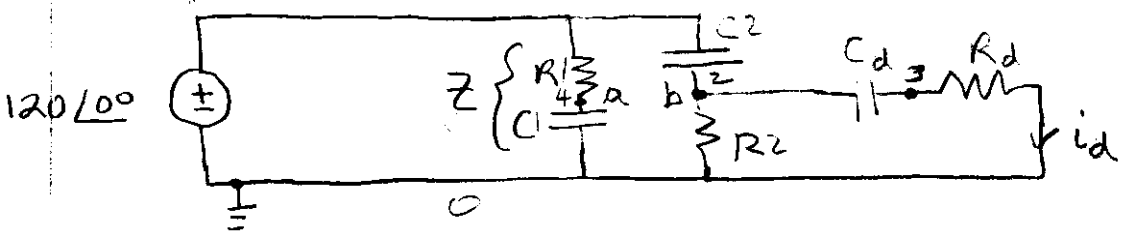14.6 Monitor hazard current is the current (i_d) that flows through the detector when one of the isolated conductors in the F.T. is grounded:



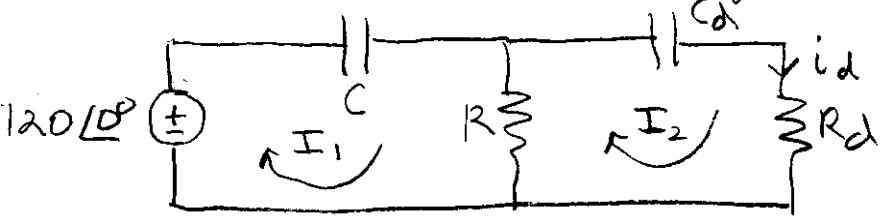note Z doesn't affect i_d since it is parallel to the voltage source:



$$120 = \frac{1}{j\omega C} I_1 + R(I_1 - I_2)$$

$$120 = I_1 \left(R + \frac{1}{j\omega C} \right) + I_2 (-R) \quad (1)$$

* assuming no other devices plugged into IT.

$$0 = I_2 \left(\frac{1}{j\omega C_d} + R_d \right) + R(I_2 - I_1)$$


$$0 = +I_1(-R) + I_2(R + R_d + \frac{1}{j\omega C_d}) \quad (2)$$

$$I_{2b} = \frac{\begin{vmatrix} R + \frac{1}{j\omega C} & 120 \\ -R & 0 \end{vmatrix}}{\begin{vmatrix} R + \frac{1}{j\omega C} & -R \\ -R & R + R_d + \frac{1}{j\omega C_d} \end{vmatrix}}$$

$$= \frac{120R}{(R + \frac{1}{j\omega C})(R + R_d + \frac{1}{j\omega C_d}) - R^2}$$

$$= \frac{120R}{R^2 + RR_d + \frac{R}{j\omega C_d} + \frac{R}{j\omega C} + \frac{R_d}{j\omega C} - \frac{1}{\omega^2 C C_d} - R^2} = i_d \quad (3)$$

now try position a:

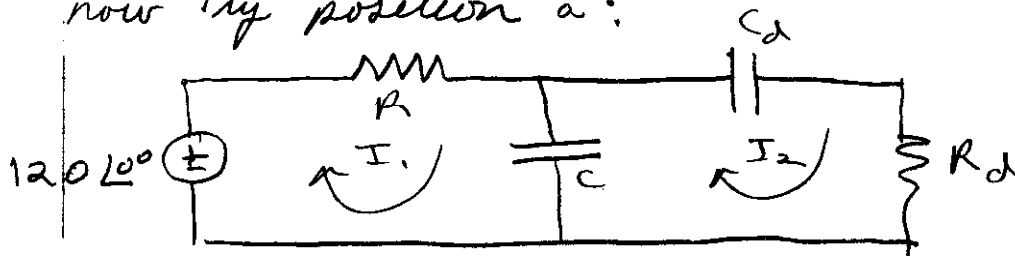

loop 1:

$$120 = I_1(R) + \frac{1}{j\omega C}(I_1 - I_2)$$

$$120 = (R + \frac{1}{j\omega C})I_1 - \frac{1}{j\omega C}I_2$$

loop 2:

$$0 = (\frac{1}{j\omega C_d} + R_d)I_2 + \frac{1}{j\omega C}(I_2 - I_1)$$

$$0 = -\frac{1}{j\omega C}I_1 + (\frac{1}{j\omega C_d} + \frac{1}{j\omega C} + R_d)I_2$$

$$I_{2a} = \begin{vmatrix} R + \frac{1}{j\omega C} & 120 \\ -\frac{1}{j\omega C} & 0 \end{vmatrix}$$

$$\begin{vmatrix} R + \frac{1}{j\omega C} & -\frac{1}{j\omega C} \\ -\frac{1}{j\omega C} & (R_d + \frac{1}{j\omega C_d} + \frac{1}{j\omega C}) \end{vmatrix}$$

$$= \frac{120/j\omega C}{(R + \frac{1}{j\omega C})(R_d + \frac{1}{j\omega C_d} + \frac{1}{j\omega C}) + \frac{1}{\omega^2 C C_d}}$$

$$= \frac{120/j\omega C}{RR_d + \frac{R}{j\omega C_d} + \frac{R}{j\omega C} + \frac{R_d}{j\omega C} - \frac{1}{\omega^2 C C_d}}$$

$$= \frac{120}{j\omega R R_d C + R \frac{C}{C_d} + R + R_d - \frac{j}{\omega C_d}}$$

$$= \frac{120 C_d}{j\omega R R_d C C_d + R C + (R + R_d) C_d - \frac{j}{\omega}}$$

$$= \frac{120 C_d}{j\omega R R_d C C_d + R C + (R + R_d) C_d - \frac{j}{\omega}} = i_d \text{ (4)}$$

Lets try tweaking R_d in (3) + (4) until $\min(I_{2a}, I_{2b}) = 25 \mu A$. This is hard to do analytically. It's easier to write a short computer program that evaluates $I_{2a} + I_{2b}$ for different values of R_d :

```
clear;
% position b current

w=60*2*pi;
R=10000;
C=0.3E-6;
Cd=0.01E-6;

for jj=1:1000

%Rd=33000;
Rd=input('enter Rd: ');
Rd=Rd*1000000;

i2b=120*R/(Rd*(R+1/(i*w*C))+R/(i*w*Cd)+R/(i*w*C)-1/(w^2*C*Cd));
abs(i2b)

%position a current

i2a=120*Cd/(Cd*(R+Rd)+R*C+i*w*R*Rd*C*Cd-i/w);
abs(i2a)

end
```

$$\underline{R_d = 3.165 M\Omega} \text{ gives } |I_{2a}| = 24.989 \mu A$$

$$|I_{2b}| = 28.262 \mu A$$

-you can also use SPICE.


Total hazard index: The total hazard index is defined as the total current, in milliamperes, that would flow to ground through a low-impedance fault if it were connected between either isolated conductor and ground. The total hazard index is made up of two components: the monitor hazard index and the fault hazard index. A LIM is usually set to alarm for a total hazard index of 2 mA.

Monitor hazard index: The monitor hazard index is the hazard current due to the LIM with no other devices plugged into the isolated power transformer.

Fault hazard index: The fault hazard index is the hazard current of a given isolated system with all devices connected except the LIM.

14.9

Circuit

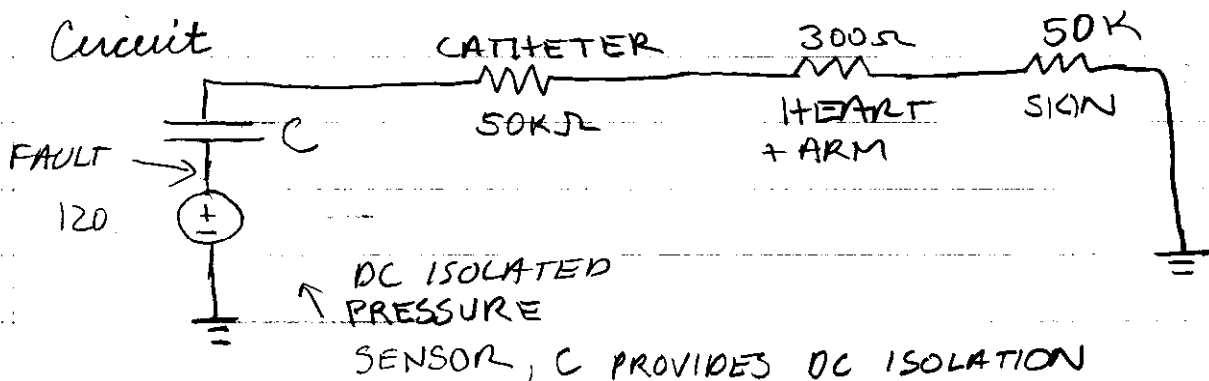

$$I_{MAX} = 10 \mu A = \frac{120}{|50K + 300 + 50K + \frac{1}{j\omega C}|}$$

$$= \frac{120}{\dots}$$

$$\left[(100.3K)^2 + \left(\frac{1}{2\pi \times 60C} \right)^2 \right]^{1/2}$$


$$(100.3K)^2 + \left(\frac{1}{120\pi C} \right)^2 = \left(\frac{120}{10^{-5}} \right)^2$$

$$\left[(120\pi C)^{-2} \right]^{-1/2} = \left[(120 \times 10^5)^2 - (100.3K)^2 \right]^{-1/2}$$

$$C = \frac{1}{\left[(120 \times 10^5)^2 - (100.3K)^2 \right]^{1/2} 120\pi} = 221 \text{ pF}$$

NOTE R HAS LITTLE EFFECT ON ANSWER

14.17)

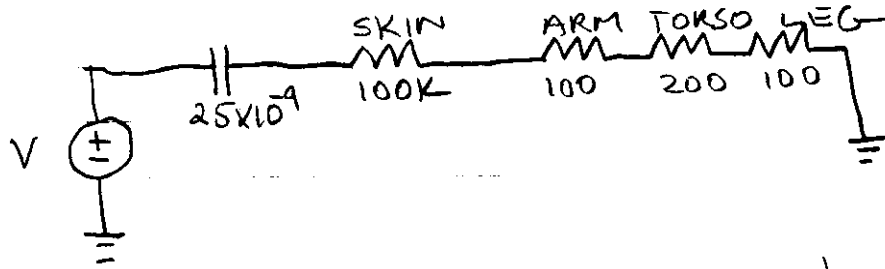

$$V = \left| \frac{1}{j(2\pi \times 60) \times 25 \times 10^{-9}} + 100.5K \right| \times 0.075$$

$$= \left| -j7,957.74 + 7,537.5 \right|$$

$$\hat{=} 10,961 \text{ V}$$