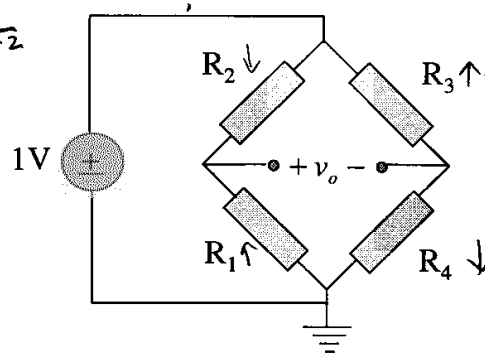


### EE 5340 Exam I

1. Each resistor in the resistive bridge forms part of an unbonded strain gauge. At equilibrium, each resistance is ~~10~~  $R$ . Assume each resistance is cylindrically shaped, and has a diameter of 1 mm, a length of 10 mm, and a resistivity of  $1 \Omega\text{-mm}$ . Determine the sensitivity in V/mm of the unbonded strain gauge. Assume resistivity and resistor diameter remain constant during stretching.

$$R = \frac{\rho L}{A} = \frac{10}{\pi r^2}$$



$$\begin{aligned} R_1 &= R + \Delta R \\ R_2 &= R - \Delta R \\ R_3 &= R + \Delta R \\ R_4 &= R - \Delta R \end{aligned}$$

$$\begin{aligned} v_o &= \frac{R_1}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \\ &= \frac{R + \Delta R}{2R} - \frac{R - \Delta R}{2R} = \frac{\Delta R}{R} \end{aligned}$$

$$\Delta R = \frac{\rho \Delta L}{A} = \frac{\Delta L}{\pi r^2}$$

$$v_o = \frac{\Delta R}{R} = \frac{\Delta L / \pi r^2}{10 / \pi r^2} = \frac{\Delta L}{10}$$

$$\text{SENSITIVITY} = \frac{\Delta v_o}{\Delta L} = \frac{1}{10} \text{ V/mm}$$

<sup>1</sup> I hereby agree to abide by the terms of the Honor Code at Southern Methodist University.

2. A thermistor  $R_T$  is linearized with a parallel resistor,  $R_p$ . The operating temperature of the linearized sensor is  $T_m = 310^\circ\text{K}$ . Assume that  $\beta = 3000^\circ\text{K}$ , and  $R_0 = 1000\ \Omega$  at  $T_0 = 298^\circ\text{K}$ . (a) Determine  $R_p$ . (b) Find the sensitivity of the linearized sensor at  $T_m$ .

$$R_{eq} = \frac{R_p R_T}{R_p + R_T} \quad , \quad R_p = R_{T_m} \frac{\beta - 2T_m}{\beta + 2T_m}$$

$$T_m = 310^\circ\text{K}$$

$$R_T = R_0 e^{\beta \left( \frac{1}{T} - \frac{1}{T_0} \right)} \quad ; \quad R_{T_m} = 10^3 e^{3000 \left( \frac{1}{310} - \frac{1}{298} \right)}$$

$$= 677.3\ \Omega$$

$$\text{a) } R_p = 677.3 \frac{(3000 - 2 \times 310)}{(3000 + 2 \times 310)}$$

$$= \underline{\underline{445.3\ \Omega}}$$

$$\text{b) SENSITIVITY OF } R_T = \frac{dR_T}{dT} = R_0 \beta \left( -1/T^2 \right) e^{\beta \left( \frac{1}{T} - \frac{1}{T_0} \right)}$$

$$= \frac{-R_0 \beta}{T^2} e^{\beta \left( \frac{1}{T} - \frac{1}{T_0} \right)}$$

$$\left. \frac{dR_T}{dT} \right|_{T=T_m} = \frac{-1000 \times 3000}{310^2} e^{3000 \left( \frac{1}{310} - \frac{1}{298} \right)}$$


$$= -21.1\ \Omega/\text{K} = R'_T$$

$$\text{SENSITIVITY OF } R'_T = \frac{(R_p + R_T) R_p R'_T + R_p R_T (R'_T)}{(R_p + R_T)^2} \Big|_{T=T_m}$$


$$= \frac{(445.3 + 677.3)(445.3)(-21.1) + 677.3(445.3)(-21.1)}{(445.3 + 677.3)^2}$$

$$= -13.4\ \Omega/\text{K}$$

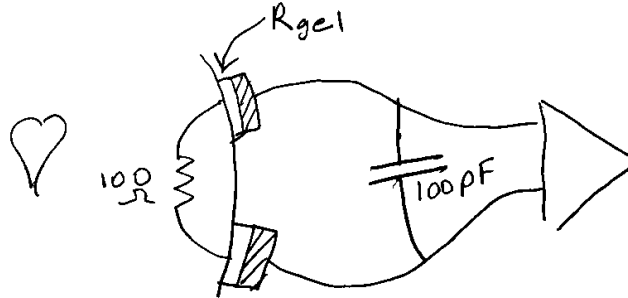4. Suppose that two ideal non-polarizable EKG electrodes are positioned on the chest. The electrodes have a surface area of  $1 \text{ cm}^2$ . Assume that the electrolyte gel occupies a  $1 \text{ mm}$  thick layer and has a resistivity of  $100 \Omega\text{-cm}$ . The tissue resistance between the electrodes can be modeled with a  $100 \Omega$  resistor. The electrode leads have zero resistance but there exists a  $100 \text{ pF}$  parasitic capacitance between them. Determine the impedance between the two electrode leads and sketch a Bode plot of the impedance as a function of frequency.


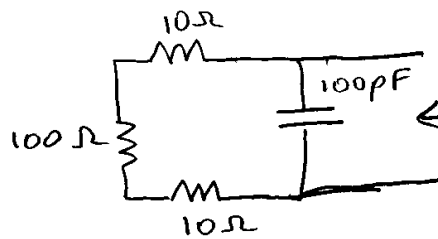
$$R_{gel} = \frac{100 \Omega\text{-cm} \times 0.1 \text{ cm}}{1 \text{ cm}^2} = 10 \Omega$$



$$Z = \frac{1}{j\omega C} \cdot 120 = \frac{120}{120 + 1/j\omega C} = \frac{120}{1 + j\omega \cdot 120 C}$$

$$= \frac{120}{1 + j\omega \cdot 120 \times 10^{-10}}$$

$$= \frac{120}{1 + j\frac{\omega}{\omega_c}}$$

$$\omega_c = \frac{1}{120 \times 10^{-10}} = 8.33 \times 10^7 \text{ RAD/S}$$

