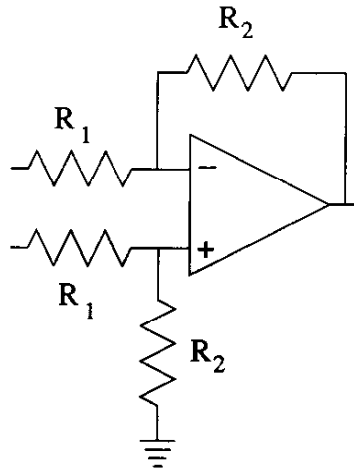


Name: _____
 October 24, 1996
 Instructor: C. Davila


EACH PROBLEM WORTH
 10 POINTS.
 MEAN = 42.9/60

SOLUTIONS
EE 5345 Midterm Exam

1. Find an expression for the input impedance Z_{in} for the differential amplifier shown below:



Assume the OP amp is ideal.

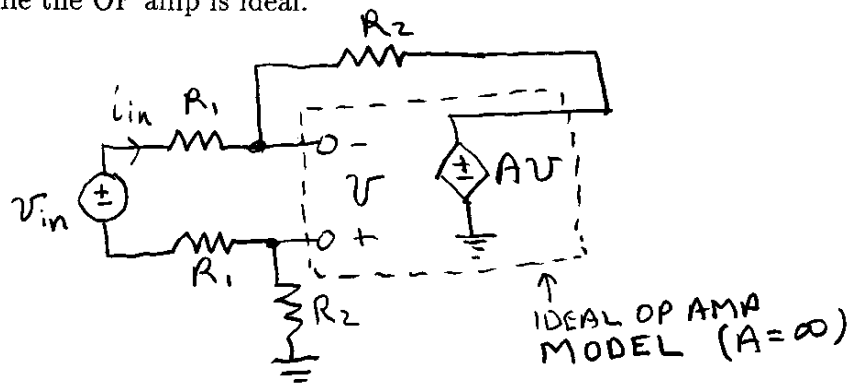

KVL: $V_{in} = 2(R_1 + R_2)i_{in} + AV$

$V = 2R_1 i_{in} - V_{in}$

$\Rightarrow V_{in} = 2(R_1 + R_2)i_{in} + A(2R_1 i_{in} - V_{in})$


$V_{in}(1+A) = [2(R_1 + R_2) + A(2R_1)]i_{in}$

$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{2(R_1 + R_2) + A(2R_1)}{1+A} \rightarrow \underline{\underline{2R_1}}$

2. Find an expression for the transfer function

$$H(j\Omega) = \frac{V_o(j\Omega)}{V_i(j\Omega)}$$




then sketch a Bode plot (dB vs $\log \Omega$) of $|H(j\Omega)|$ for $R_1 = 10k\Omega$, $R_2 = 30k\Omega$, and $C = 1\mu F$.

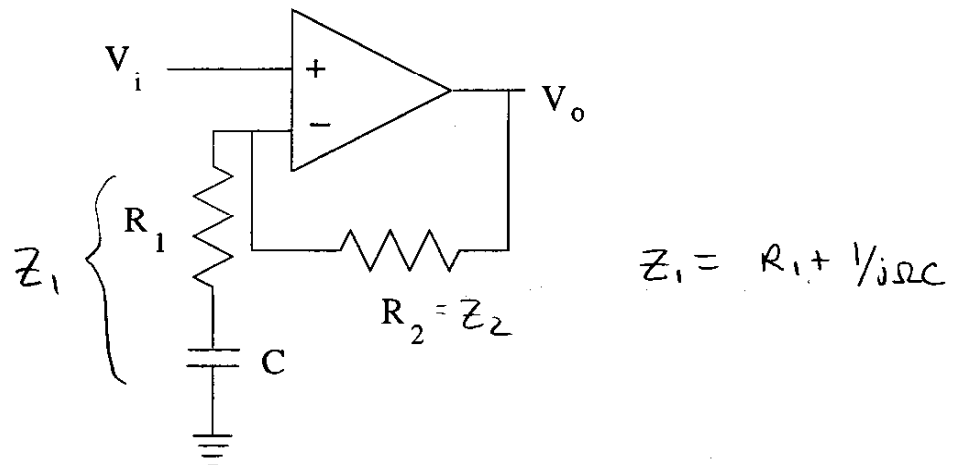


$$\frac{V_o}{V_i} = \frac{Z_1 + Z_2}{Z_1} = \frac{R_1 + 1/j\Omega C + R_2}{R_1 + 1/j\Omega C} = \frac{1 + j\Omega(R_1 + R_2)C}{1 + j\Omega R_1 C}$$

$$H(j\Omega) = \frac{1 + j\Omega/\Omega_1}{1 + j\Omega/\Omega_2} \quad \Omega_1 = \frac{1}{(R_1 + R_2)C} = 25 \text{ rad/s}$$

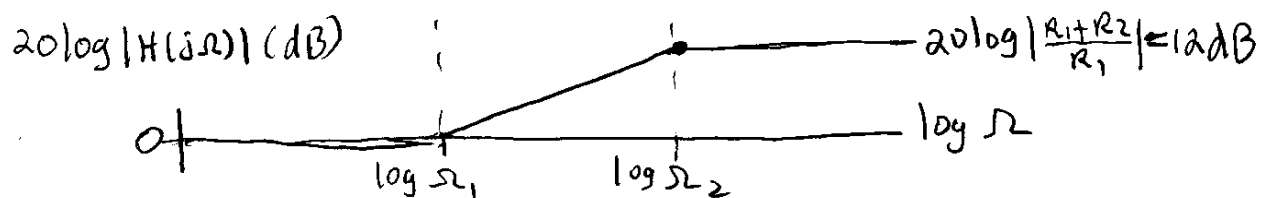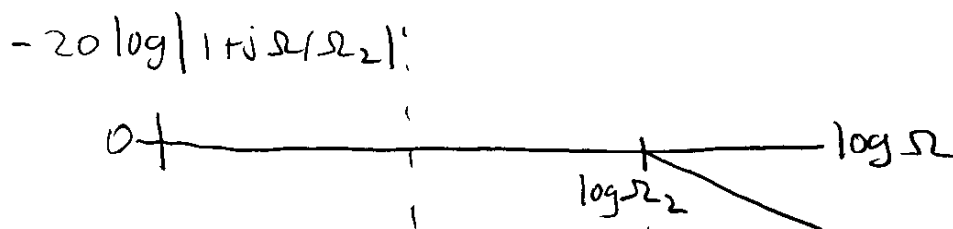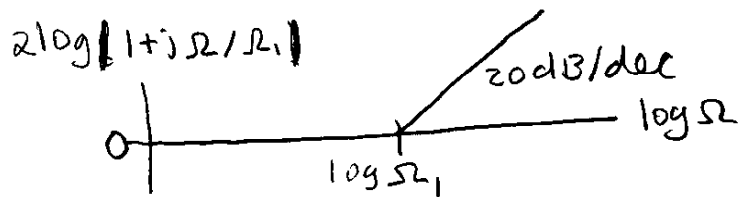
$$\Omega_2 = \frac{1}{R_1 C} = 100 \text{ rad/s}$$



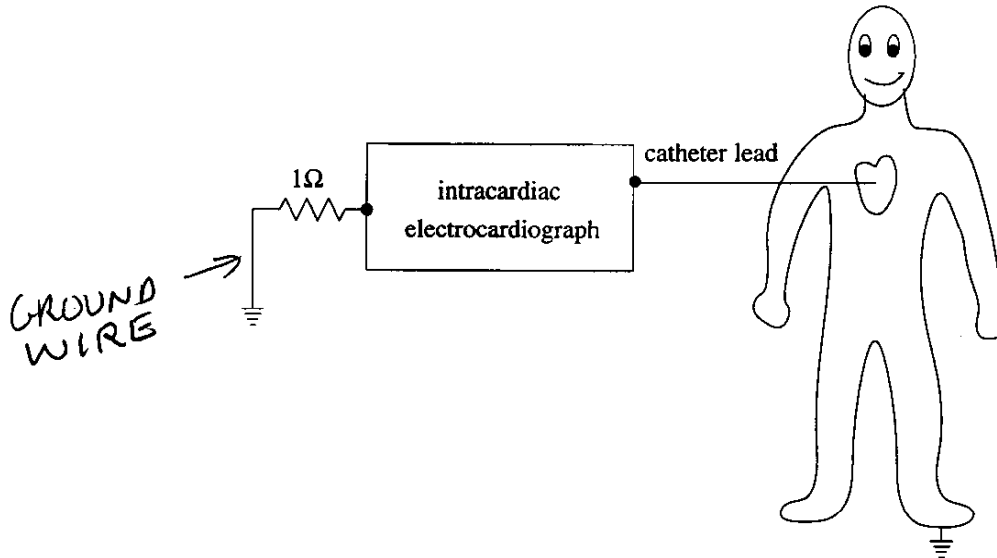3. A technician measures the leakage current between the chassis and ground on an intracardiac electrocardiograph and finds it to be $200\mu A$. The electrocardiograph has a 0-resistance intracardiac lead connected to the chassis. This lead is subsequently connected to a patient's heart in the ICU. The patient touches a grounded object as shown. Make appropriate assumptions about tissue resistances, and determine whether a microshock hazard exists. Fully justify your answer.



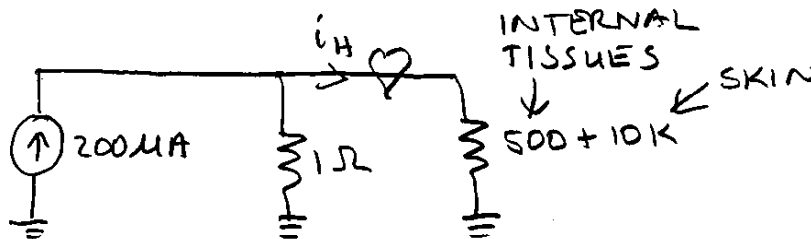THE $200\mu A$ LEAKAGE CURRENT HAS 2 PATHS TO GROUND, THROUGH GROUND WIRE + THROUGH HEART:



$$i_H = \frac{200 \times 10^{-6} \times 1}{1 + 10.5 \times 10^3} = 1.9 \times 10^{-8} < 10 \mu A$$

SO THERE IS NO HAZARD

IF GROUND WIRE BREAKS \rightarrow MICROSHOCK

4. A digital lowpass filter has transfer function:

$$H(z) = \frac{1}{1 - 0.9z^{-1}}$$

Find the output of the filter, $y[n]$, $n = 0, \dots, 4$ for the input $x = \{\underbrace{1}_{n=0}, -1\}$. Assume that $y[n] = 0$ for $n < 0$.

$$y[n] = 0.9y[n-1] + x[n]$$

$$y[0] = 0.9 \times 0 + 1 = 1$$

$$y[1] = 0.9 - 1 = -0.1$$

$$y[2] = 0.9(-0.1) = -0.09$$

$$y[3] = 0.9(-0.09) = -0.081$$

$$y[4] = 0.9(-0.081) = -0.0729$$

5. Design a digital filter using the bilinear transform method that meets the following specifications:

- $T = 10^{-4} \text{ s}$
- $|H(j\Omega)| = -3 \text{ dB}, \Omega = 1200\pi \text{ rad/s} = \Omega_c$
- $|H(j\Omega)| < -10 \text{ dB}, \Omega > 4000\pi \text{ rad/s} = \Omega_a$

write down the filter difference equation.

$$\omega_c = \Omega_c T = 0.12\pi$$

$$\omega_a = \Omega_a T = 0.4\pi$$

PREWARP:

$$\Omega'_c = \frac{z}{T} \tan\left(\frac{\omega_c}{z}\right) = \frac{z}{T} 0.1908$$

$$\Omega'_a = \frac{z}{T} \tan\left(\frac{\omega_a}{z}\right) = \frac{z}{T} 0.7265$$

$$N = \frac{\log(10^{10/10} - 1)}{2 \log\left(\frac{0.7265}{0.1908}\right)} = 0.8217 \rightarrow 1$$

$$H^R(s) = \frac{1}{B_1(s)} = \frac{1}{s+1}$$

$$H(s) = H^R\left(\frac{s}{\Omega'_c}\right) = \frac{\Omega'_c}{s + \Omega'_c}$$

$$H(z) = H(s) \Big|_{s = \frac{z}{T} \frac{1-z^{-1}}{1+z^{-1}}}$$

$$= \frac{\Omega'_c}{\frac{z}{T} \frac{1-z^{-1}}{1+z^{-1}} + \Omega'_c} = \frac{\frac{T}{z} \Omega'_c (1+z^{-1})}{1-z^{-1} + \frac{T}{z} \Omega'_c (1+z^{-1})}$$


$$= \frac{0.1908 (1+z^{-1})}{1.1908 + (0.1908-1)z^{-1}} = \frac{0.1908 (1+z^{-1})}{1 + \frac{(0.1908-1)z^{-1}}{1.1908}}$$

$$= \frac{0.1602 (1+z^{-1})}{1 - 0.6795 z^{-1}}$$


$$y[n] = 0.6795 y[n-1] + 0.1602 (x[n] + x[n-1])$$

6. Briefly describe 4 different types of tests that measure leakage current in clinical electrophysiology instruments.


1. CHASSIS LEAKAGE CURRENT

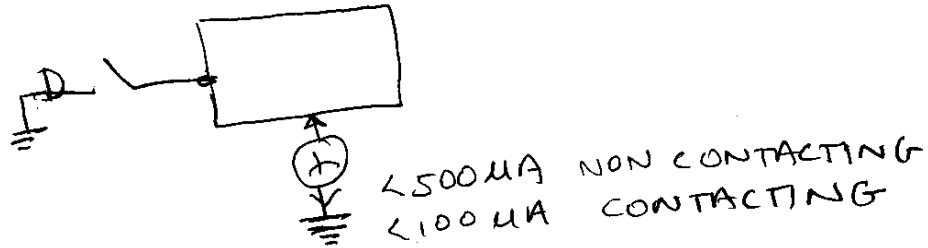

2. PATIENT LEAD TO GROUND

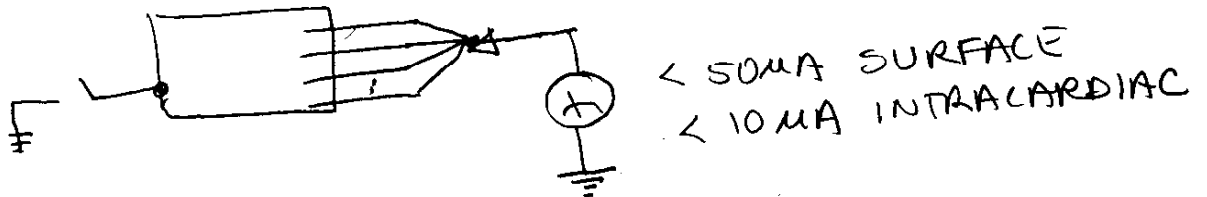

3. BETWEEN PATIENT LEADS

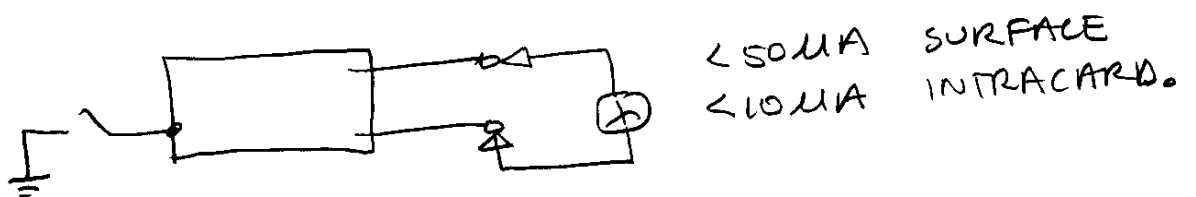

4. TESTS SHOULD BE REPEATED W/ CHASSIS GROUNDED,