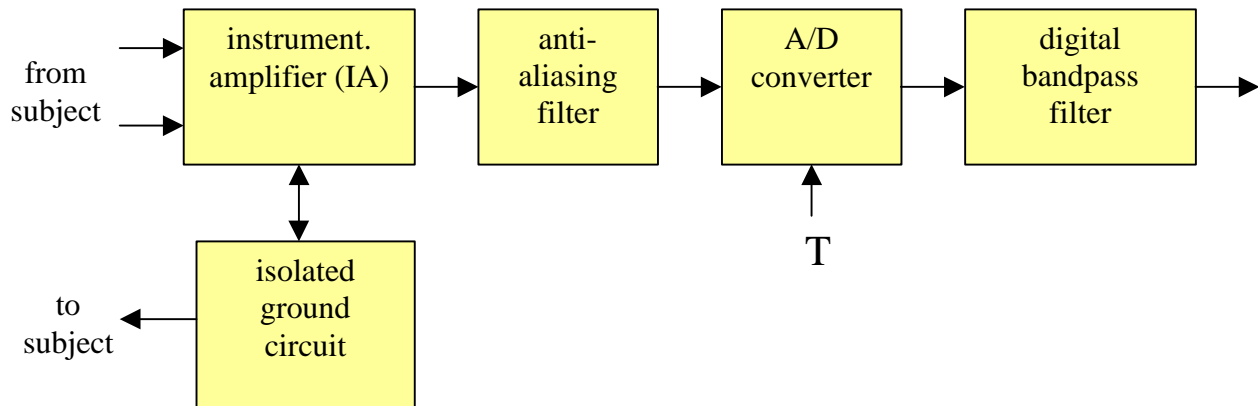


The exam concerns the following block diagram for measuring an EEG signal:



1. Design an instrumentation amplifier for measuring an EEG signal, the desired output should be 5 volts, typically (see Table 1 of Webster) and the IA should have high CMRR. Also design an isolated ground circuit that provides a grounding point to the subject while keeping him isolated from earth ground. Why is isolation from ground important?
2. Design an anti-aliasing (lowpass) 2-pole analog filter that cuts off at 30 Hz. Use a single operational amplifier. What is the gain of the filter at 0 Hz? What is the gain of the filter at 30 Hz?
3. Determine the sampling interval T such that the signal level at one half the sampling rate has been attenuated by 0.01 relative to the gain of the anti-aliasing filter at 0 Hz.
4. Determine what operation should be applied to the coefficients of an FIR lowpass filter to convert it to a bandpass filter. Hint: use the frequency shifting property of the Fourier Transform (i.e. multiplication of $h[n]$ by $\exp(j\omega_0 n)$ produces a certain frequency shift in $H(e^{j\omega})$).
5. Use the result of the previous problem to design a 5-tap FIR bandpass filter that has a passband between 0.2π and 0.6π radians.


SOLUTIONS

1. FROM TABLE 1.1 : TYPICAL AMPLITUDE OF EEG IS 100 μ V

WANT TO BOOST THIS TO 5V SO

$$A_d = \frac{5V}{100 \times 10^{-6}V} = 5 \times 10^4$$

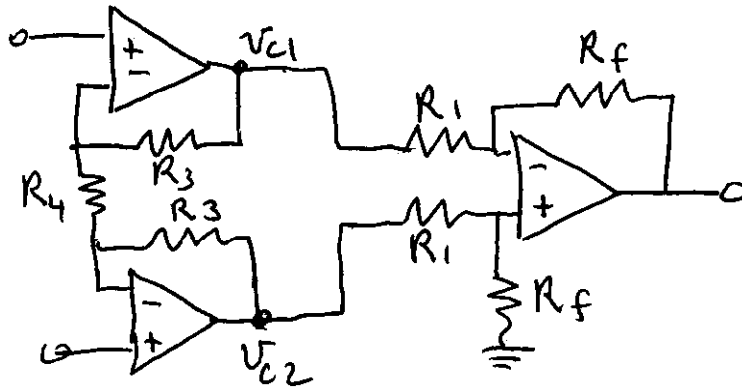WE MUST DESIGN OUR AMP TO HAVE A DIFFERENTIAL GAIN OF 50,000.



$$A_d = \frac{R_f}{R_1} \left(\frac{2R_3 + R_4}{R_4} \right)$$


ANY COMBINATION WORKS

$$R_3 = 22K\Omega \quad R_4 = 1K\Omega \Rightarrow \left(\frac{2R_3 + R_4}{R_4} \right) = 45$$

$$R_f = 1000K\Omega \quad R_1 = 900\Omega$$


= 1M Ω WOULD DO IT (ASSUMING IDEAL OP AMPS)

ISOLATION! USE DRIVEN RIGHT LEG CIRCUIT!

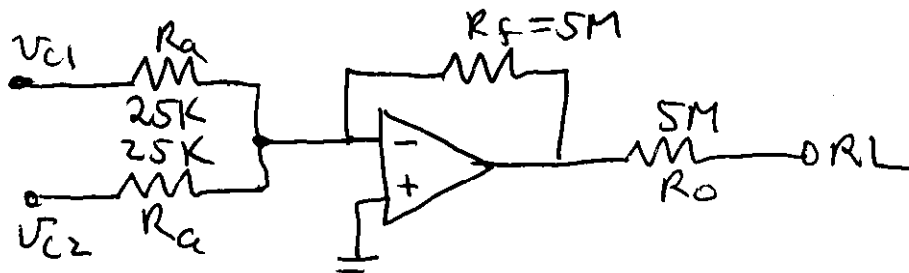

ISOLATION IS IMPORTANT BECAUSE IT PREVENTS A PATIENT FROM PROVIDING A PATH TO GROUND FOR CURRENT.

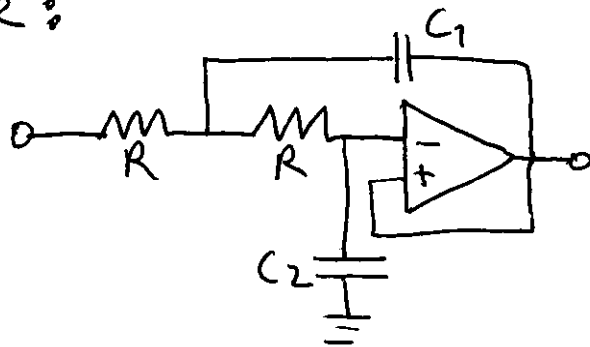2. ANTI-ALIASING FILTER IS A LOWPASS FILTER:



$$\Omega_c = 2\pi \times 30 = 60\pi$$

PICK $R = 10\text{K}\Omega$

$$C_1 = \frac{\sqrt{2}}{R\Omega_c} = \frac{\sqrt{2}}{10^4 \times 60\pi} \doteq 0.75 \mu\text{F}$$

$$C_2 = \frac{1}{\sqrt{2}R\Omega_c} = \frac{1}{\sqrt{2} \times 10^4 \times 60\pi} \doteq 0.375 \mu\text{F}$$

GAIN OF FILTER AT 0 Hz = 0dB OR 1
 GAIN OF " " 30Hz = -3dB OR $1/\sqrt{2}$

- THIS IS TRUE OF ALL BUTTERWORTH FILTERS.

3. WE NOW SEEK SAMPLING INTERVAL T SO THAT $|H(j\Omega_N)| = 0.01$ WHERE $\Omega_N = \frac{1}{2}$ SAMPLING FREQ.
 $= \frac{1}{2} \cdot \frac{2\pi}{T} = \frac{\pi}{T}$

$$H(j\Omega_N) = \frac{1}{1 - \left(\frac{\Omega_N}{\Omega_c}\right)^2 + j\sqrt{2}\left(\frac{\Omega_N}{\Omega_c}\right)}$$

$$|H(j\Omega_N)|^2 = \frac{1}{1 + \left(\frac{\Omega_N}{\Omega_c}\right)^4} = 10^{-4}$$

$$10^4 = 1 + \left(\frac{\Omega_N}{\Omega_c}\right)^4 \quad \rightarrow \quad \Omega_N = \Omega_c (10^4 - 1)^{1/4} = \frac{\pi}{T}$$

$$\rightarrow \frac{\Omega_N}{\Omega_c} = (10^4 - 1)^{1/4} \quad \rightarrow \quad T = \frac{\pi}{60\pi (10^4 - 1)^{1/4}} = 0.0016667$$


4. FREQ. SHIFTING PROPERTY:

IF $\tilde{H}\{h[n]\} = H(e^{j\omega})$


THEN

$$\begin{aligned} \tilde{H}\{e^{+j\omega_0 n} h[n]\} &= \sum_{n=-\infty}^{\infty} h[n] e^{j\omega_0 n} e^{-j\omega n} \\ &= \sum_{n=-\infty}^{\infty} h[n] e^{-j(\omega - \omega_0)n} \\ &= H(e^{j(\omega - \omega_0)}) \end{aligned}$$


SO IF $H(e^{j\omega})$ IS LOW PASS:

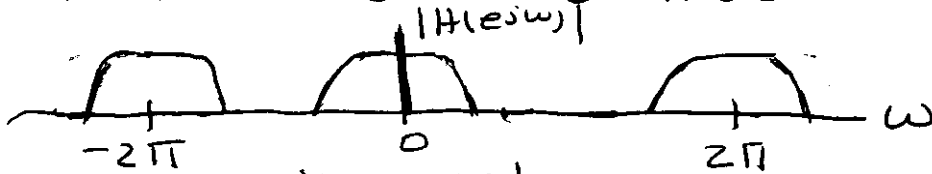

THEN $|H(e^{j(\omega - \omega_0)})|$ LOOKS LIKE:

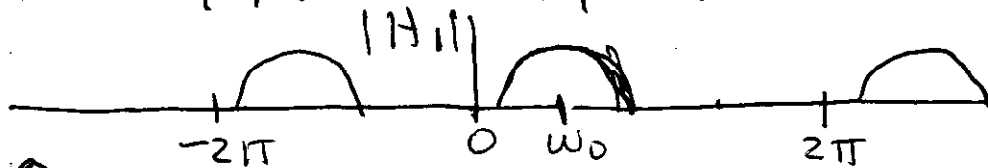

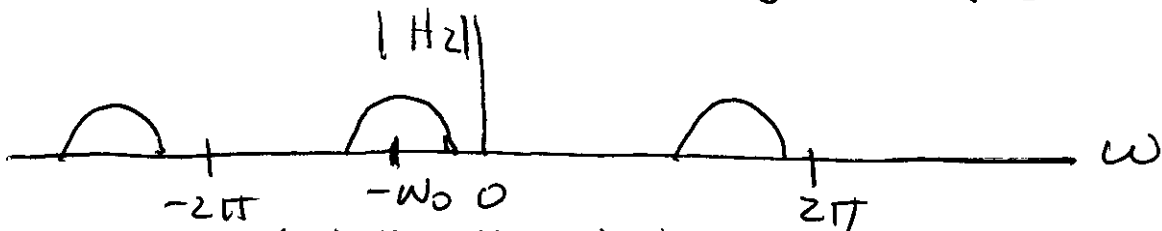↑ THIS IS TECHNICALLY A BANDPASS FILTER BUT IT DOESN'T HAVE REAL COEFFICIENTS WHICH IS DESIREABLE, SO BETTER TO ALSO SHIFT BY $+\omega_0$ ($e^{-j\omega_0 n} h[n]$)



ADDING $H_1(e^{j\omega}) + H_2(e^{j\omega})$ GIVES:




WHICH HAS THE FORM OF A BANDPASS FILTER AS SEEN ON SLIDE 139. IN TIME DOMAIN


$$h_3[n] = h[n] (e^{j\omega_0 n} + e^{-j\omega_0 n})$$

$$\uparrow \text{BP} \quad = 2h[n] \cos \omega_0 n$$

S. WANT:

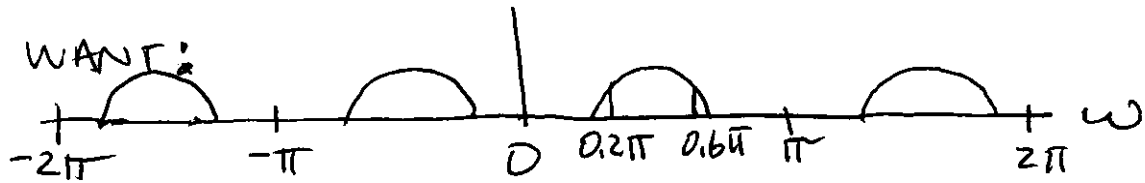

START WITH:

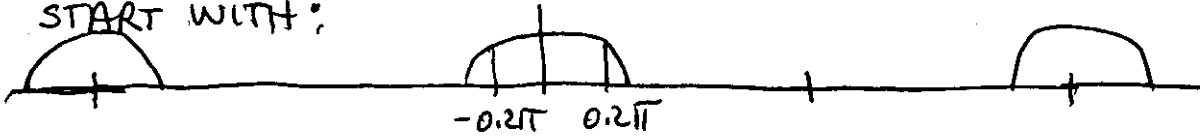

$$\Rightarrow \omega_0 = 0.4\pi$$

NOW DESIGN LOWPASS FILTER:

$$h_{LP}[n] = \frac{\sin(n \cdot 0.2\pi)}{\pi n} \quad n = 0, \pm 1, \pm 2$$

$$h_{BP}[n] = 2h_{LP}[n] \cos(0.4\pi n)$$