


# ECE 2350 **CIRCUIT** ANALYSIS I

**Homework 2**  
28 January 2020


**Professor Dunham**  
**Due: 4 February 2020**

Review Lecture Notes.

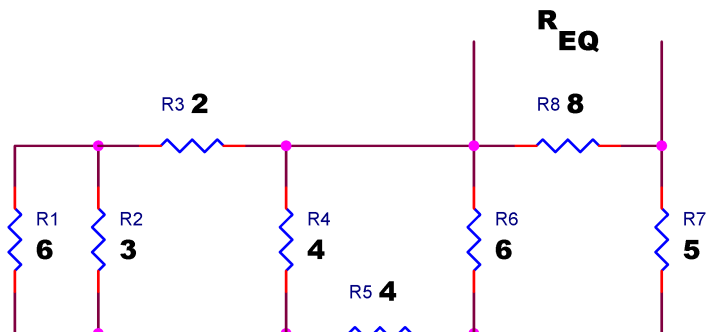
1. Find the equivalent resistance  $R_{eq}$  in the circuit below.



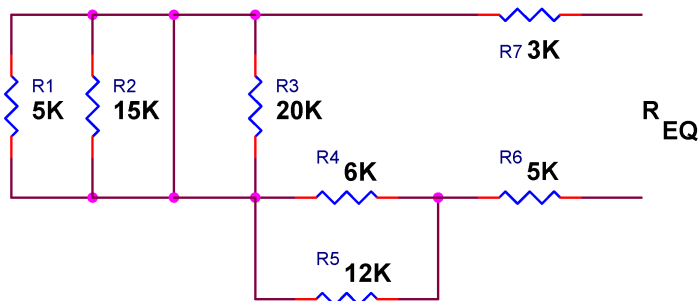
2. Find the equivalent resistance  $R_{eq}$  in the circuit below.



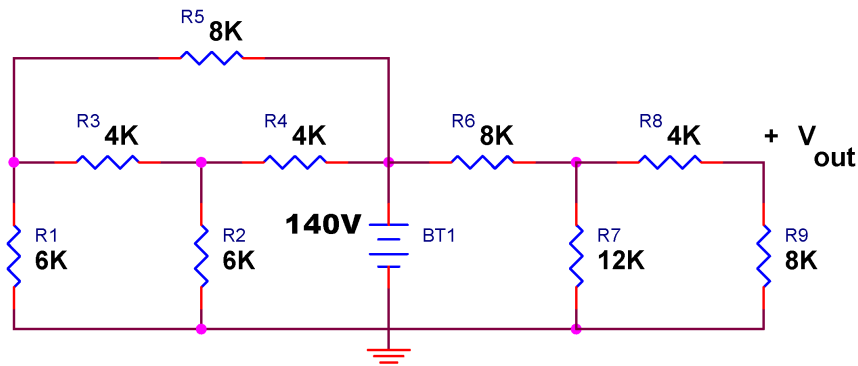
3. Use the voltage divider formula to find the voltage  $V_{out}$  in the circuit below. *Hint:* Focus on the relevant part of the circuit to solve the problem.



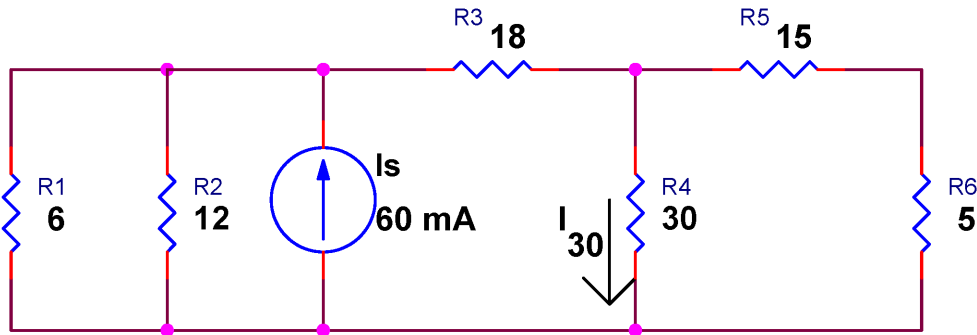4. Use the current divider formula to find the current  $I_{30}$  in the circuit below.



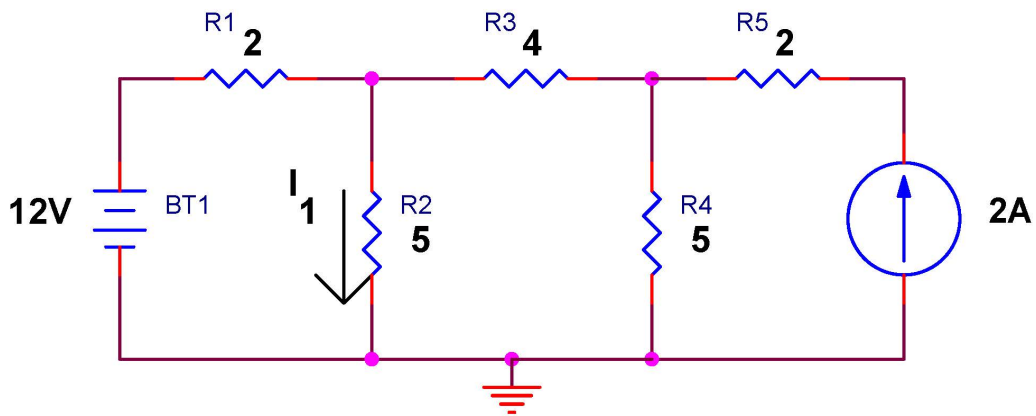5. Use a loop analysis method to find current  $I_1$  in the circuit below. Identify all the nodal voltages in the circuit and specify their values using 3 decimal points of accuracy.



6. In the circuit below use a loop analysis to specify the voltage source  $V_S$  so that 20 watts of power are dissipated in the  $5\Omega$  resistor. Be sure to provide both solutions.

