

## Binary Storage

- Binary Cell: A Device that Possesses Two Stable States
- Cell Input: Receives Data and Control Signals that Set it to One of the States
- Cell Output: Physical Quantity Indicating Which State the Cell is in
- States are Encoded as Binary Digits {0,1}

## Registers

- Group of  $n$  Binary Cells: an  $n$ -bit Register
- Register has  $2^n$  States: All Possible  $n$ -bit Strings
- Register State (or content) can be *INTERPRETED* as a Value, ASCII, etc.
- Registers Classified as to Type of Input and Output – Serial and/or Parallel

*Much More on This Later in the Class*

## Register Transfer

- General Way to Describe a Digital Circuit (including a computer)
- Registers are Interconnected
- At a Given Time Content of One Register *Transferred* to Another
- Content May be *Transformed/Changed* During Transfer
- Transforming Circuit is a *Data Processing* or *Data Path* Element/Circuit

## Register Transfer (cont)

- General Way to Describe a Digital Circuit
  - Can Use Diagrams
  - Can Use *Register Transfer Languages*
- Register Transfer Descriptions are Often the First Descriptions Developed in Design Process
- Example: Keyboard to Registers to Memory
  - Key Strike: 8-bit ASCII to Right-most Register
  - Key Strike: Register Content Shifted Left
  - 4 Key Strikes: Content Transferred to Memory

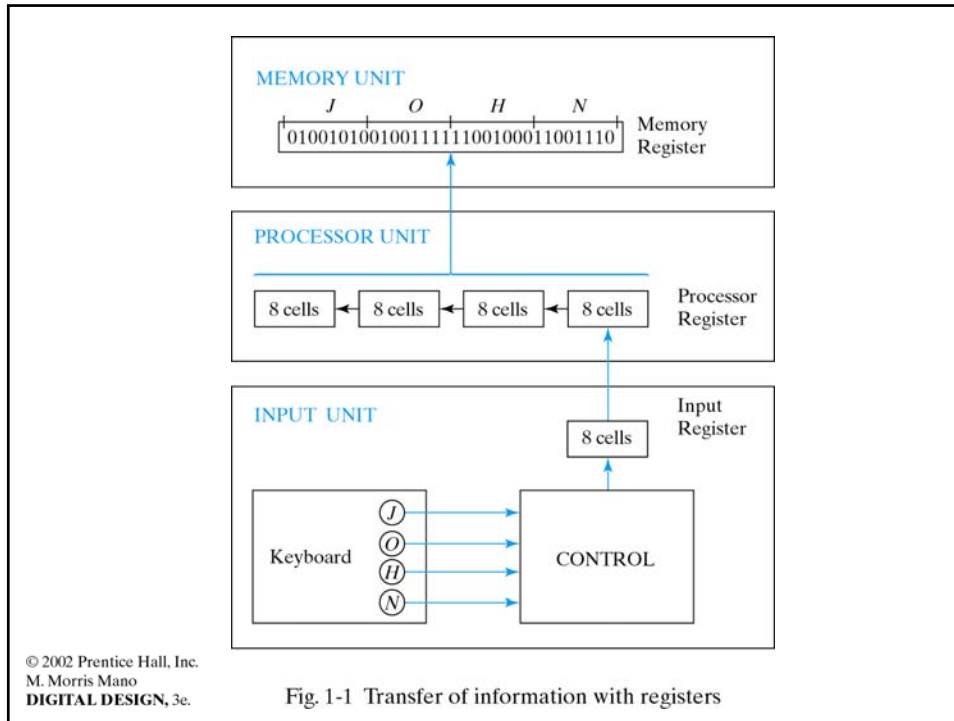


Fig. 1-1 Transfer of information with registers

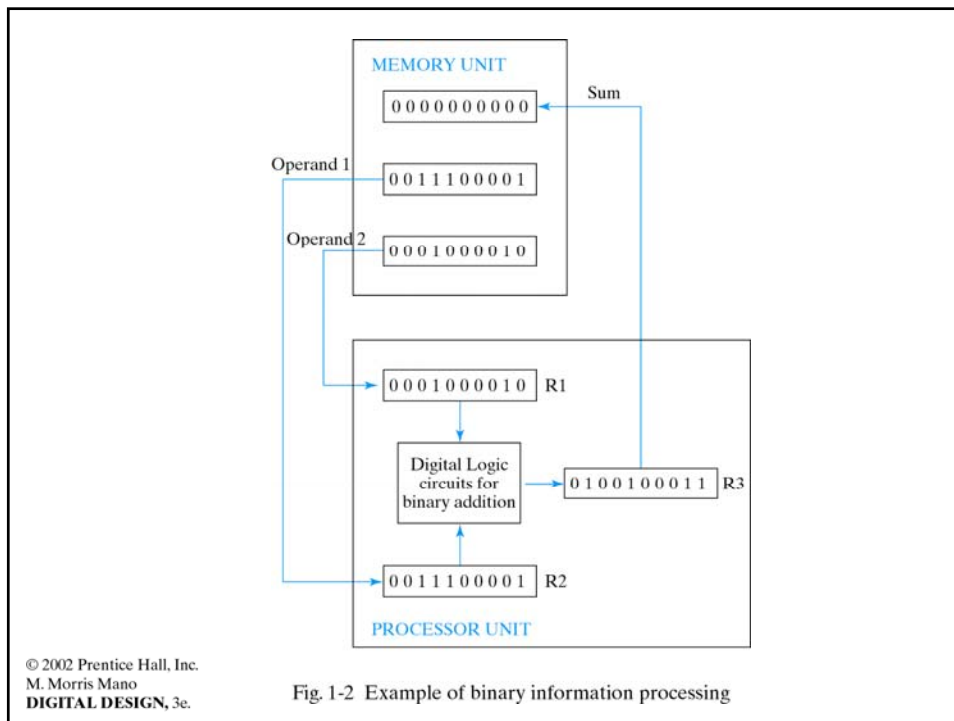


Fig. 1-2 Example of binary information processing

## Binary Logic

- Deals With Variables that have Two Different Values – Typically BITS {0,1}
- Logic is Based on *Boolean Algebra* Operators
- Boolean Algebra DOES NOT Necessarily Have to Be Based on Binary Values
- Formal Introduction in Following Sections

## Binary Logic

- Variables Denoted by Letters of Alphabet
  - *EXAMPLES*  
 $A, B, C, a, b, c, x_1, x_2, x_3, \text{ etc.}$
- Three Basic Operations Considered (for now)
  - AND (Boolean Algebra Multiplication)
  - OR (Boolean Algebra Addition)
  - NOT (Boolean Algebra Inversion)

## Binary AND Operation

- Represented by a Dot • **OR** Absence of Operator Between Adjacent Variables or Constants

$$x \bullet y = z \quad xy = z$$

$x$  AND  $y$  is equal to  $z$

$z=1$  if and only if  $x$  AND  $y = 1$ ,  
otherwise  $z=0$

- Truth Table Definition:

$x$	$y$	$x \bullet y$
0	0	0
0	1	0
1	0	0
1	1	1

## Binary OR Operation

- Represented by a Plus Sign + Between Adjacent Variables or Constants

$$x + y = z$$

$x$  OR  $y$  is equal to  $z$

$z=1$  if  $x=1$  OR  $y=1$  OR both  $x=y=1$ ,  
otherwise  $z=0$

- Truth Table Definition:

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

## Binary NOT Operation

- Represented by a Prime Sign ' OR an Overbar
- Unary Operator – Operates on One Variable

$$x' = z \qquad \bar{x} = z$$

NOT  $x$  is equal to  $z$


if  $x=1$  THEN  $z=0$  ELSE both  $z=1$

- Truth Table Definition:

$x$	$z = \bar{x}$
0	1
1	0
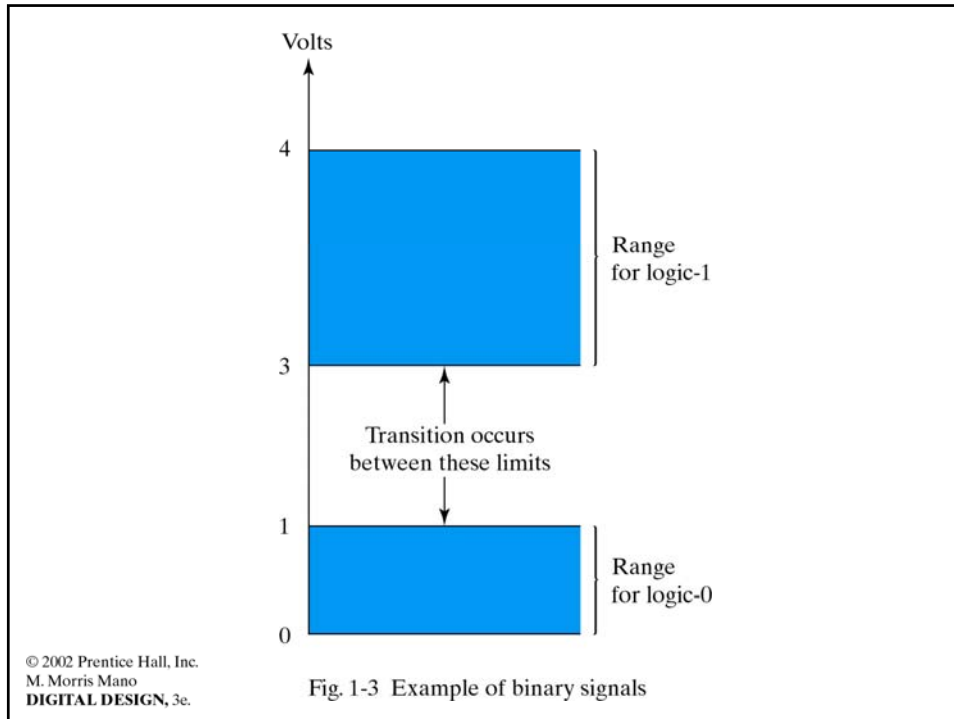
## Logic Gates

- Electronic Circuits Operate on 1 or More Input Signals
- Produce an Output Signal Corresponding to a Boolean Operation
- Signals are Voltages or Currents
- Signals Interpreted as a 0 or 1
- Defined by a Range of Voltage or Current Values



## Logic Gates

- Circuit Diagrams Use Graphical Symbols for Logic Gates
- Connections of Logic Gates Between Registers can Transform Data
- Logic Gates Represent Interconnections of Transistors and Other Electronic Components


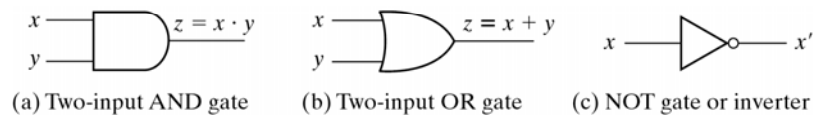


Fig. 1-4 Symbols for digital logic circuits
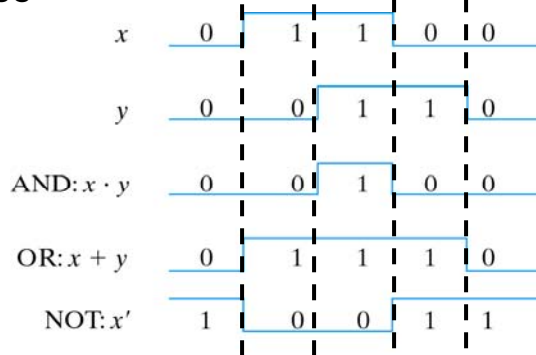
## Timing Diagrams

- Depict Input and Output Signals as Functions of Time
- Values Toggle Between Two Discrete Values



© 2002 Prentice Hall, Inc.  
M. Morris Mano  
DIGITAL DESIGN, 3e.

Fig. 1-5 Input-output signals for gates

## Multi-input Logic Gates

- Many Logic Gates Can Have More than Two Inputs
- Examples are AND and OR Gates

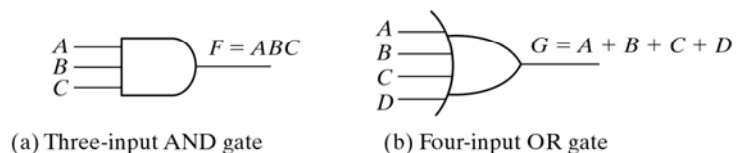


Fig. 1-6 Gates with multiple inputs

© 2002 Prentice Hall, Inc.  
M. Morris Mano  
DIGITAL DESIGN, 3e.